
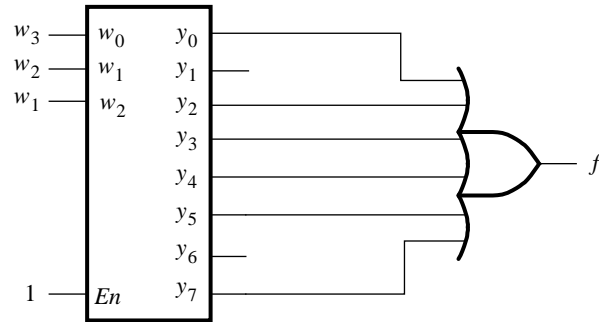


# Chapter 6


6.1.

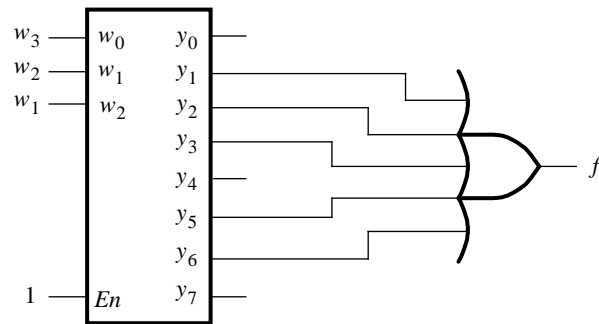

6.2.



6.3.

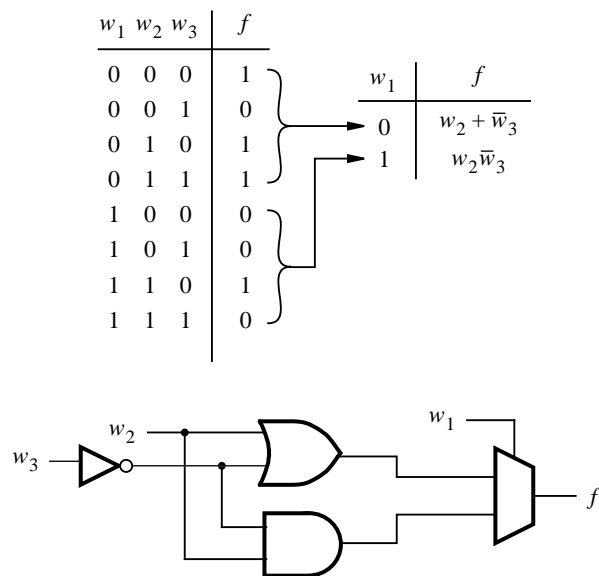


6.4.

$w_1$	$w_2$	$w_3$	$f$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$w_1$	$f$
0	$\bar{w}_2\bar{w}_3$
1	$w_2 + \bar{w}_3$

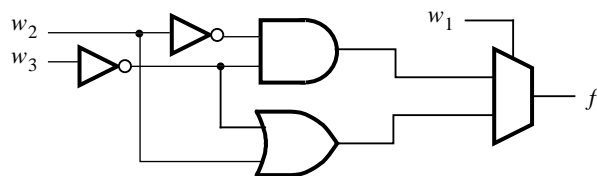


6.5. The function  $f$  can be expressed as

$$f = \bar{w}_1\bar{w}_2\bar{w}_3 + \bar{w}_1w_2\bar{w}_3 + \bar{w}_1w_2w_3 + w_1w_2\bar{w}_3$$

Expansion in terms of  $w_1$  produces

$$f = \bar{w}_1(w_2 + \bar{w}_3) + w_1(w_2\bar{w}_3)$$

The corresponding circuit is

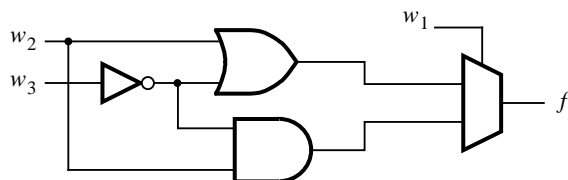


6.6. The function  $f$  can be expressed as

$$f = \bar{w}_1\bar{w}_2\bar{w}_3 + w_1\bar{w}_2\bar{w}_3 + w_1w_2\bar{w}_3 + w_1w_2w_3$$

Expansion in terms of  $w_2$  produces

$$f = \bar{w}_2(\bar{w}_3) + w_2(w_1)$$

The corresponding circuit is

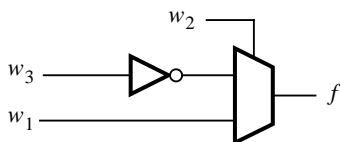

6.7. Expansion in terms of  $w_2$  gives

$$\begin{aligned} f &= \bar{w}_2(1 + \bar{w}_1\bar{w}_3 + w_1w_3) + w_2(\bar{w}_1\bar{w}_3 + w_1w_3) \\ &= \bar{w}_1\bar{w}_2\bar{w}_3 + w_1\bar{w}_2w_3 + \bar{w}_2 + \bar{w}_1w_2\bar{w}_3 + w_1w_2w_3 \end{aligned}$$

Further expansion in terms of  $w_1$  gives

$$\begin{aligned} f &= \bar{w}_1(w_2\bar{w}_3 + \bar{w}_2\bar{w}_3 + \bar{w}_2) + w_1(w_2w_3 + \bar{w}_2w_3 + \bar{w}_2) \\ &= \bar{w}_1w_2\bar{w}_3 + \bar{w}_1\bar{w}_2\bar{w}_3 + \bar{w}_1\bar{w}_2 + w_1w_2w_3 + w_1\bar{w}_2w_3 + w_1\bar{w}_2 \end{aligned}$$

Further expansion in terms of  $w_3$  gives

$$\begin{aligned} f &= \bar{w}_3(\bar{w}_1w_2 + \bar{w}_1\bar{w}_2 + \bar{w}_1\bar{w}_2 + w_1\bar{w}_2) + w_3(w_1w_2 + w_1\bar{w}_2 + w_1\bar{w}_2 + \bar{w}_1\bar{w}_2) \\ &= \bar{w}_1w_2\bar{w}_3 + \bar{w}_1\bar{w}_2\bar{w}_3 + w_1\bar{w}_2\bar{w}_3 + w_1w_2w_3 + w_1\bar{w}_2w_3 + \bar{w}_1\bar{w}_2w_3 \end{aligned}$$

6.8. Expansion in terms of  $w_1$  gives

$$f = \bar{w}_1w_2 + \bar{w}_1\bar{w}_3 + w_1w_2$$

Further expansion in terms of  $w_2$  gives

$$\begin{aligned} f &= \bar{w}_2(\bar{w}_1\bar{w}_3) + w_2(w_1 + \bar{w}_1 + \bar{w}_1\bar{w}_3) \\ &= \bar{w}_1w_2 + \bar{w}_1w_2\bar{w}_3 + \bar{w}_1\bar{w}_2\bar{w}_3 + w_1w_2 \end{aligned}$$

Further expansion in terms of  $w_3$  gives

$$\begin{aligned} f &= \bar{w}_3(\bar{w}_1\bar{w}_2 + w_1w_2 + \bar{w}_1w_2 + \bar{w}_1w_2) + w_3(w_1w_2 + \bar{w}_1w_2) \\ &= \bar{w}_1\bar{w}_2\bar{w}_3 + w_1w_2\bar{w}_3 + \bar{w}_1w_2\bar{w}_3 + \bar{w}_1w_2w_3 + w_1w_2w_3 \end{aligned}$$

6.9. Proof of Shannon's expansion theorem

$$f(x_1, x_2, \dots, x_n) = \bar{x}_1 \cdot f(0, x_2, \dots, x_n) + x_1 \cdot f(1, x_2, \dots, x_n)$$

This theorem can be proved using *perfect induction*, by showing that the expression is true for every possible value of  $x_1$ . Since  $x_1$  is a boolean variable, we need to look at only two cases:  $x_1 = 0$  and  $x_1 = 1$ .

Setting  $x_1 = 0$  in the above expression, we have:

$$\begin{aligned} f(0, x_2, \dots, x_n) &= 1 \cdot f(0, x_2, \dots, x_n) + 0 \cdot f(1, x_2, \dots, x_n) \\ &= f(0, x_2, \dots, x_n) \end{aligned}$$

Setting  $x_1 = 1$ , we have:

$$\begin{aligned} f(1, x_2, \dots, x_n) &= 0 \cdot f(0, x_2, \dots, x_n) + 1 \cdot f(1, x_2, \dots, x_n) \\ &= f(1, x_2, \dots, x_n) \end{aligned}$$

This proof can be performed for any arbitrary  $x_i$  in the same manner.

6.10. Derivation using  $\bar{f}$ :

$$\begin{aligned} \bar{f} &= \bar{w}\bar{f}_{\bar{w}} + w\bar{f}_w \\ f &= \overline{\bar{w}\bar{f}_{\bar{w}} + w\bar{f}_w} \\ &= \overline{\bar{w}\bar{f}_{\bar{w}}} \cdot \overline{w\bar{f}_w} \\ &= (w + f_{\bar{w}})(\bar{w} + f_w) \end{aligned}$$


6.11. Expansion in terms of  $w_2$  gives

$$f = \overline{w}_2(\overline{w}_1 + \overline{w}_3) + w_2(w_1w_3)$$

Letting  $g = \overline{w}_1 + \overline{w}_3$ , we have

$$f = \overline{w}_2g + w_2\overline{g}$$

The corresponding circuit is

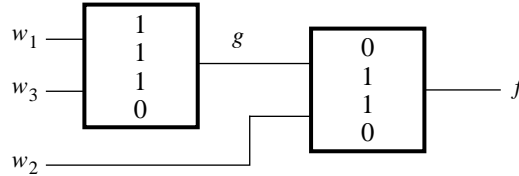

6.12. Expansion of  $f$  in terms of  $w_2$  gives

$$\begin{aligned} f &= \overline{w}_2(\overline{w}_1 + \overline{w}_3) + w_2(w_1w_3) \\ &= w_2 \oplus (\overline{w}_1 + \overline{w}_3) \\ &= w_2 \oplus \overline{w}_1\overline{w}_3 \end{aligned}$$

The cost of this multilevel circuit is 2 gates + 4 inputs = 6.

6.13. Using Shannon's expansion in terms of  $w_2$  we have

$$\begin{aligned} f &= \overline{w}_2(\overline{w}_3 + \overline{w}_1w_4) + w_2(w_3\overline{w}_4 + w_1w_3) \\ &= \overline{w}_2(\overline{w}_3 + \overline{w}_1w_4) + w_2(w_3(w_1 + \overline{w}_4)) \end{aligned}$$

If we let  $g = \overline{w}_3 + \overline{w}_1w_4$ , then

$$f = \overline{w}_2g + w_2\overline{g}$$

Thus, two 3-LUTs are needed to implement  $f$ .


6.14. Any number of 5-variable functions can be implemented by using two 4-LUTs. For example, if we cascade the two 4-LUTs by connecting the output of one 4-LUT to an input of the other, then we can realize any function of the form

$$\begin{aligned} f &= f_1(w_1, w_2, w_3, w_4) + w_5 \\ f &= f_1(w_1, w_2, w_3, w_4) \cdot w_5 \end{aligned}$$

 6.15. Shannon's expansion with respect to  $w_1$  and  $w_2$  gives

$$\begin{aligned}
 f &= \overline{w_1}\overline{w_2}\overline{w_4}\overline{w_5} + w_1w_2 + w_1w_3 + w_1w_4 + w_3w_4w_5 \\
 &= \overline{w_1}\overline{w_2}f_{\overline{w_1}\overline{w_2}} + \overline{w_1}w_2f_{\overline{w_1}w_2} + w_1\overline{w_2}f_{w_1\overline{w_2}} + w_1w_2f_{w_1w_2} \\
 &= \overline{w_1}\overline{w_2}(\overline{w_4}\overline{w_5} + w_3w_4w_5) + \overline{w_1}w_2(w_3w_4w_5) + w_1\overline{w_2}(w_3 + w_4) + w_1w_2(1)
 \end{aligned}$$


Since only uncomplemented inputs are available, the term  $\overline{w_4}\overline{w_5}$  has to be implemented as  $\overline{w_4 + w_5}$ . The resulting circuit is



6.16. Using Shannon's expansion in terms of  $w_3$  we have

$$\begin{aligned}
 f &= \overline{w_3}(w_2) + w_3(w_1 + \overline{w_2}) \\
 &= \overline{w_3}(w_2) + w_3(\overline{w_2} + w_2w_1)
 \end{aligned}$$


The corresponding circuit is

 

6.17. Using Shannon's expansion in terms of  $w_3$  we have

$$f = w_3(\bar{w}_1 + w_1\bar{w}_2) + \bar{w}_3(w_1 + \bar{w}_1w_2)$$

The corresponding circuit is

 

6.18. The code in Figure P6.2 is a 2-to-4 decoder with an enable input. It is not a good style for defining this decoder. The code is not easy to read. Moreover, the VHDL compiler often turns **if** statements into multiplexers, in which case the resulting decoder may have multiplexers controlled by the  $En$  signal on the output side.

```
6.19.    LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

        ENTITY prob6_19 IS
            PORT ( w : IN  STD_LOGIC_VECTOR(1 TO 3) ;
                  f : OUT STD_LOGIC ) ;
        END prob6_19 ;

        ARCHITECTURE Behavior OF prob6_19 IS
        BEGIN
            WITH w SELECT
                f <= '0' WHEN "001",
                  '0' WHEN "110",
                  '1' WHEN OTHERS ;
        END Behavior ;
```

```

6.20.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

        ENTITY prob6_20 IS
            PORT ( w : IN  STD_LOGIC_VECTOR(1 TO 3) ;
                  f : OUT STD_LOGIC ) ;
        END prob6_20 ;

        ARCHITECTURE Behavior OF prob6_20 IS
        BEGIN
            WITH w SELECT
                f <= '0' WHEN "000",
                  '0' WHEN "100",
                  '0' WHEN "111",
                  '1' WHEN OTHERS ;
        END Behavior ;

6.21.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

        ENTITY prob6_21 IS
            PORT ( w : IN  STD_LOGIC_VECTOR(3 DOWNTO 0) ;
                  y : OUT STD_LOGIC_VECTOR(1 DOWNTO 0) ) ;
        END prob6_21 ;

        ARCHITECTURE Behavior OF prob6_21 IS
        BEGIN
            WITH w SELECT
                y <= "00" WHEN "0001",
                  "01" WHEN "0010",
                  "10" WHEN "0100",
                  "11" WHEN OTHERS ;
        END Behavior ;

6.22.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

        ENTITY prob6_22 IS
            PORT ( w : IN  STD_LOGIC_VECTOR(7 DOWNTO 0) ;
                  y : OUT STD_LOGIC_VECTOR(2 DOWNTO 0) ) ;
        END prob6_22 ;

        ... con't

```

```

ARCHITECTURE Behavior OF prob6_22 IS
BEGIN
    y <= "000" WHEN w = "00000001" ELSE
        "001" WHEN w = "00000010" ELSE
        "010" WHEN w = "00000100" ELSE
        "011" WHEN w = "00001000" ELSE
        "100" WHEN w = "00010000" ELSE
        "101" WHEN w = "00100000" ELSE
        "110" WHEN w = "01000000" ELSE
        "111";
END Behavior ;

```

6.23. First define a set of intermediate variables

$$\begin{aligned}
 i_0 &= \overline{w_7}\overline{w_6}\overline{w_5}\overline{w_4}\overline{w_3}\overline{w_2}\overline{w_1}w_0 \\
 i_1 &= \overline{w_7}\overline{w_6}\overline{w_5}\overline{w_4}\overline{w_3}\overline{w_2}w_1 \\
 i_2 &= \overline{w_7}\overline{w_6}\overline{w_5}\overline{w_4}\overline{w_3}w_2 \\
 i_3 &= \overline{w_7}\overline{w_6}\overline{w_5}\overline{w_4}w_3 \\
 i_4 &= \overline{w_7}\overline{w_6}\overline{w_5}w_4 \\
 i_5 &= \overline{w_7}\overline{w_6}w_5 \\
 i_6 &= \overline{w_7}w_6 \\
 i_7 &= w_7
 \end{aligned}$$

Now a traditional binary encoder can be used for the priority encoder

$$\begin{aligned}
 y_0 &= i_1 + i_3 + i_5 + i_7 \\
 y_1 &= i_2 + i_3 + i_6 + i_7 \\
 y_2 &= i_4 + i_5 + i_6 + i_7
 \end{aligned}$$

```

6.24.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

ENTITY prob6_24 IS
    PORT ( w : IN  STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          y : OUT STD_LOGIC_VECTOR(2 DOWNTO 0) ;
          z : OUT STD_LOGIC ) ;
END prob6_24 ;

ARCHITECTURE Behavior OF prob6_24 IS
BEGIN
    y <= "111" WHEN w(7) = '1' ELSE
        "110" WHEN w(6) = '1' ELSE
        "101" WHEN w(5) = '1' ELSE
        "100" WHEN w(4) = '1' ELSE
        "011" WHEN w(3) = '1' ELSE
        "010" WHEN w(2) = '1' ELSE
        "001" WHEN w(1) = '1' ELSE
        "000";
    z <= '0' WHEN w="00000000" ELSE '1' ;
END Behavior ;

```



```

6.25.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

        ENTITY prob6_25 IS
            PORT ( w : IN  STD_LOGIC_VECTOR(7 DOWNTO 0) ;
                  y : OUT STD_LOGIC_VECTOR(2 DOWNTO 0) ;
                  z : OUT STD_LOGIC ) ;
        END prob6_25 ;

        ARCHITECTURE Behavior OF prob6_25 IS
        BEGIN
            PROCESS ( w )
            BEGIN
                IF w(7) = '1' THEN
                    y <= "111" ;
                ELSIF w(6) = '1' THEN
                    y <= "110" ;
                ELSIF w(5) = '1' THEN
                    y <= "101" ;
                ELSIF w(4) = '1' THEN
                    y <= "100" ;
                ELSIF w(3) = '1' THEN
                    y <= "011" ;
                ELSIF w(2) = '1' THEN
                    y <= "010" ;
                ELSIF w(1) = '1' THEN
                    y <= "001" ;
                ELSE
                    y <= "000" ;
                END IF ;
                IF w = "00000000" THEN
                    z <= '0' ;
                ELSE
                    z <= '1' ;
                END IF ;
            END PROCESS ;
        END Behavior ;

6.26.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

        ENTITY if2to4 IS
            PORT ( w : IN  STD_LOGIC_VECTOR(1 DOWNTO 0) ;
                  En : IN  STD_LOGIC ;
                  y : OUT STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
        END if2to4 ;

        ... con't

```

ARCHITECTURE Behavior OF if2to4 IS

BEGIN

    PROCESS ( En, w )

    BEGIN

        IF En = '0' THEN

            y <= "0000";

        ELSE

            IF w = "00" THEN

                y <= "0001";

            ELSIF w = "01" THEN

                y <= "0010";

            ELSIF w = "10" THEN

                y <= "0100";

            ELSE

                y <= "1000";

            END IF;

        END IF;

    END PROCESS;

END Behavior;

LIBRARY ieee;

USE ieee.std\_logic\_1164.all;

PACKAGE if2to4\_package IS

    COMPONENT if2to4

        PORT ( w : IN STD\_LOGIC\_VECTOR(1 DOWNTO 0);

            En : IN STD\_LOGIC;

            y : OUT STD\_LOGIC\_VECTOR(3 DOWNTO 0) );

    END COMPONENT;

END if2to4\_package;

LIBRARY ieee;

USE ieee.std\_logic\_1164.all;

USE work.if2to4\_package.all;

ENTITY h3to8 IS

    PORT ( w : IN STD\_LOGIC\_VECTOR(2 DOWNTO 0);

            En : IN STD\_LOGIC;

            y : OUT STD\_LOGIC\_VECTOR(7 DOWNTO 0) );

END h3to8;

ARCHITECTURE Structure OF h3to8 IS

    SIGNAL EnableTop, EnableBot : STD\_LOGIC;

BEGIN

    EnableTop <= w(2) AND En;

    EnableBot <= (NOT w(2)) AND En;

    Decoder1: if2to4 PORT MAP ( w( 1 DOWNTO 0 ), EnableBot, y( 3 DOWNTO 0 ) );

    Decoder2: if2to4 PORT MAP ( w( 1 DOWNTO 0 ), EnableTop, y( 7 DOWNTO 4 ) );

END Structure;

... con't

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
PACKAGE h3to8_package IS
    COMPONENT h3to8
        PORT ( w : IN    STD_LOGIC_VECTOR(2 DOWNTO 0) ;
              En : IN    STD_LOGIC ;
              y : OUT   STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
    END COMPONENT ;
END h3to8_package ;

```

6.27.

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.h3to8_package.all ;

ENTITY h6to64 IS
    PORT ( w : IN    STD_LOGIC_VECTOR( 5 DOWNTO 0 ) ;
          En : IN    STD_LOGIC ;
          y : OUT   STD_LOGIC_VECTOR(63 DOWNTO 0) ) ;
END h6to64 ;

ARCHITECTURE Structure OF h6to64 IS
    SIGNAL Enables : STD_LOGIC_VECTOR( 7 DOWNTO 0 ) ;
BEGIN
    root : h3to8 PORT MAP ( w( 5 DOWNTO 3 ), En, Enables ) ;
    leaf0: h3to8 PORT MAP ( w( 2 DOWNTO 0 ), Enables( 0 ), y( 7 DOWNTO 0 ) ) ;
    leaf1: h3to8 PORT MAP ( w( 2 DOWNTO 0 ), Enables( 1 ), y( 15 DOWNTO 8 ) ) ;
    leaf2: h3to8 PORT MAP ( w( 2 DOWNTO 0 ), Enables( 2 ), y( 23 DOWNTO 16 ) ) ;
    leaf3: h3to8 PORT MAP ( w( 2 DOWNTO 0 ), Enables( 3 ), y( 31 DOWNTO 24 ) ) ;
    leaf4: h3to8 PORT MAP ( w( 2 DOWNTO 0 ), Enables( 4 ), y( 39 DOWNTO 32 ) ) ;
    leaf5: h3to8 PORT MAP ( w( 2 DOWNTO 0 ), Enables( 5 ), y( 47 DOWNTO 40 ) ) ;
    leaf6: h3to8 PORT MAP ( w( 2 DOWNTO 0 ), Enables( 6 ), y( 55 DOWNTO 48 ) ) ;
    leaf7: h3to8 PORT MAP ( w( 2 DOWNTO 0 ), Enables( 7 ), y( 63 DOWNTO 56 ) ) ;
END Structure ;

```

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY prob6_28 IS
    PORT ( bcd : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          leds : OUT STD_LOGIC_VECTOR(1 TO 7) ) ;
END prob6_28 ;

ARCHITECTURE Behavior OF prob6_28 IS
BEGIN
    WITH bcd SELECT
        --      abcdefg
        leds <= "1111110" WHEN "0000",
               "0110000" WHEN "0001",
               "1101101" WHEN "0010",
               "1111001" WHEN "0011",
               "0110011" WHEN "0100",
               "1011011" WHEN "0101",
               "1011111" WHEN "0110",
               "1110000" WHEN "0111",
               "1111111" WHEN "1000",
               "1111011" WHEN "1001",
               "-----" WHEN OTHERS ;
END Behavior ;

```


$$\begin{aligned} a &= w_3 + w_2 w_0 + w_1 + \overline{w}_2 \overline{w}_0 \\ b &= w_3 + \overline{w}_1 \overline{w}_0 + w_1 w_0 + \overline{w}_2 \\ c &= w_2 + \overline{w}_1 + w_0 \end{aligned}$$

$$\begin{aligned} d &= w_3 + \overline{w_2}\overline{w_0} + w_1\overline{w_0} + w_2\overline{w_1}w_0 + \overline{w_2}w_1 \\ e &= \overline{w_2}\overline{w_0} + w_1\overline{w_0} \\ f &= w_3 + \overline{w_1}\overline{w_0} + w_2\overline{w_0} + w_2\overline{w_1} \\ g &= w_3 + w_1\overline{w_0} + w_2\overline{w_1} + \overline{w_2}w_1 \end{aligned}$$


arrangement similar to Figure 6.56, the desired circuit can be specified by the following truth table:

<i>Left</i>	<i>Right</i>	$h$	$y_3$	$y_2$	$y_1$	$y_0$	$k$
0	0	0	$w_3$	$w_2$	$w_1$	$w_0$	0
0	1	0	$w_0$	$w_3$	$w_2$	$w_1$	$w_0$
1	0	$w_3$	$w_2$	$w_1$	$w_0$	$w_3$	0

 
Using multiplexers, this truth table may be realized as



 
- 6.32. (a) Each ROM location that should store a 1 requires no circuitry, because the pull-up resistor provides the default value of 1. Each location that stores a 0 has the following cell



(b)

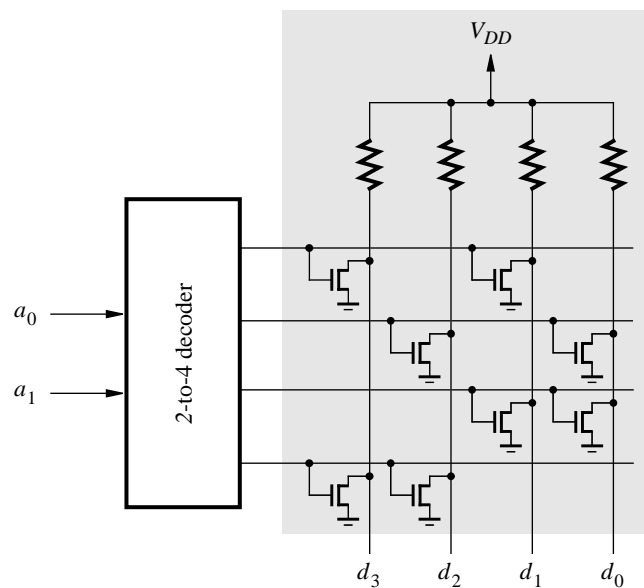

 (c) Every location in the ROM contains the following cell



If a location should store a 1, then the corresponding EEPROM transistor is programmed to be turned off. But if the location should store a 0, then the EEPROM transistor is left unprogrammed.

(d)

